



**Requirements for this paper:**

Multi choice cards: ☐

Programmable calculator: ☐

Graphic paper: ☐

Laptop: ☐

Open book examination ☐

EKSAMEN/  
EXAMINATION:

Semestertoets 1b  
Semester test 1b

KWALIFIKASIEPROGRAM/  
/QUALIFICATION PROGRAM:

MODULEKODE/  
MODULE CODE:

**EERI 423**

DUUR/  
DURATION:

**1 uur / 1**

MODULE BESKRYWING/  
MODULE DESCRIPTION:

**Telekommunikasie /  
Telecommunication**

MAKS / MAX:

**hours**

EKSAMINATOR(E)/  
EXAMINER(S):

**Prof A.S.J. Helberg**

DATUM /  
DATE:

**2017-05-02**

MODERATOR:

**Prof J.E.W. Holm**

TYD / TIME:

**12:00**

**TOTAAL / TOTAL: 20**

*Beantwoord die volgende vrae in u antwoordskrif:*

*Answer the following questions in your answerbook:*

1) 'n Superheterodene ontvanger het 'n insetsein van 14.5MHz en die plaaslike ossilator is ingestem op 19MHz.

- a) Wat is die Intermediere frekwensie? [1]
- b) Wat is die beeld frekwensie? [1]
- c) Dui die verskillende seine in die frekwensie domein aan. [2]

*A superheterodyne receiver receives an input signal of 14.5MHz while the local oscillator is tuned to 19MHz.*

- a) *What is the intermediate frequency?* [1]
- b) *What is the image frequency?* [1]
- c) *Show the different signals present in the frequency domain.* [2]

- a) **IF = 19MHz-14.5MHz = 4.5MHz** [1]
- b) **Image = 19MHz + 4.5MHz =23.5MHz** [1]
- c) **4.5MHz, 14.5MHz, 19MHz, 23.5MHz, amplitudes of IF and Image the same** [2]

2) 'n Versterker met 6ohm impedansie moet aan 'n antenna met 50ohm impedansie gekoppel word om teen 155MHz maksimum drywing te lewer. Ontwerp 'n L tipe impedansie-aanpassingsnetwerk en gee die waardes van L, C en Q vir u netwerk. [6]

*An amplifier with impedance of 6ohm must be connected to an antenna with a 50ohm impedance in such a way that the maximum power is delivered at 155MHz. Design an L-type impedance matching network and give the values of L, C and Q for your network. [6]*

### ANSWER

Suppose we wish to match a  $6\text{-}\Omega$  transistor amplifier impedance to a  $50\text{-}\Omega$  antenna load at 155 MHz. In this case,  $R_i < R_L$ , so we use the formulas in Fig. 8-38(b).

$$X_L = \sqrt{R_i R_L - (R_i)^2} = \sqrt{6(50) - (6)^2} = \sqrt{300 - 36} = \sqrt{264} = 16.25 \text{ }\Omega$$

$$Q = \sqrt{\frac{R_L}{R_i} - 1} = \sqrt{\frac{50}{6} - 1} = 2.7$$

$$X_C = \frac{R_i R_L}{X_L} = \frac{50(6)}{16.25} = 18.46 \text{ }\Omega$$

To find the values of  $L$  and  $C$  at 155 MHz, we rearrange the basic reactance formulas as follows:

$$X_L = 2\pi f L$$

$$L = \frac{X_L}{2\pi f} = \frac{16.25}{6.28 \times 155 \times 10^6} = 16.7 \text{ nH}$$

$$X_C = \frac{1}{2\pi f C}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{6.28 \times 155 \times 10^6 \times 18.46} = 55.65 \text{ pF}$$

**Regte groep formules kies = 1 punt, daarna een punt vir elke berekening  $X_C$ ,  $X_L$ ,  $Q$ ,  $L$ ,  $C$**

- 3) 'n Ontvanger met 'n  $75\text{ohm}$  insetimpedansie werk teen 'n temperatuur van 40 grade Celsius. 'n  $106\text{MHz}$  sein met 'n bandwydte van  $8\text{MHz}$  word ontvang. Die ontvangde seinsterkte van  $6\text{uV}$  versterk deur 'n versterker met 'n ruis syfer van  $3.1\text{dB}$ . Bepaal die volgende:

- a) Die ruis drywing by die inset [2]
- b) Die insetsein drywing [1]
- c) Die inset sein-tot-ruis verhouding in dB [2]
- d) Die uitset sein-tot-ruis verhouding in dB [3]
- e) Die ruis temperatuur van die versterker [1]
- f) Wat is die kleinste sein wat onderskei kan word? [1]

*A receiver with a  $75\text{ohm}$  input impedance operates at a temperature of 40 degrees Celsius. The received signal is at  $106\text{MHz}$  with a bandwidth of  $8\text{MHz}$ . The received signal voltage of  $6\text{uV}$  is applied to an amplifier with a noise figure of  $3.1\text{dB}$ . Find the following:*

- a) *input noise power* [2]
- b) *input signal power* [1]
- c) *input signal to noise ratio in dB* [2]

- d) *output signal to noise ratio in dB* [3]  
e) *noise temperature of the amplifier* [1]  
f) *What is the smallest signal that can be discerned?* [1]

<b>Question 3</b>								
Input impedance	75 Ohm							
Noise temperature	313 K	40 C					1	
Bandwidth	8.00E+06 Hz							
Noise figure	3.1 dB							
Input voltage	6.00E-06 uV							
a) Noise power (Vn)	3.2E-06 V	sqrt(4kTBR)	10log(kTB)	-1.35E+02				
Noise power (Pn)	1.38E-13						1	
b) RF power (Ps)	4.8E-13 W						1	
c) S/N ratio before	3.47 Ratio						1	
	5.4 dB	10log(ratio)					1	
d) S/N after								
Noise ratio of receiver	2.04 Ratio						1	
	1.7 Ratio	NR = c/d					1	
	2.3 dB	10log(ratio)					1	
e) Noise temperature	301.6 K	Tn = 290(NR-1)					1	
f) MDS	-102 dBm						1	
						Total		10

## FORMULES EN TABELLE/ FORMULAS AND TABLES

### Ontvangers, versenders en ruis / *Receivers, transmitters, and noise*

---

$$v_n = \sqrt{4kTBR}$$

$$P_n = kTB$$

$$k = 1.38 \times 10^{-23} \text{ J / K}$$

$$i_n = \sqrt{2qI_{DC}B}$$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$S / N = \frac{P_s}{P_n}$$


$$NR = NR_1 + \frac{NR_2 - 1}{A_{P1}} + \frac{NR_3 - 1}{A_{P1} \cdot A_{P2}} + \frac{NR_4 - 1}{A_{P1} \cdot A_{P2} \cdot A_{P3}} + \dots$$

$$T_N = 290 (NR - 1)$$

$$R = MN + A \quad NR = \frac{S / N_{INPUT}}{S / N_{OUTPUT}}$$

$$MDS = -174dBm + 10\log(B) + NF$$

**Figure 8-39** The L network design equations.

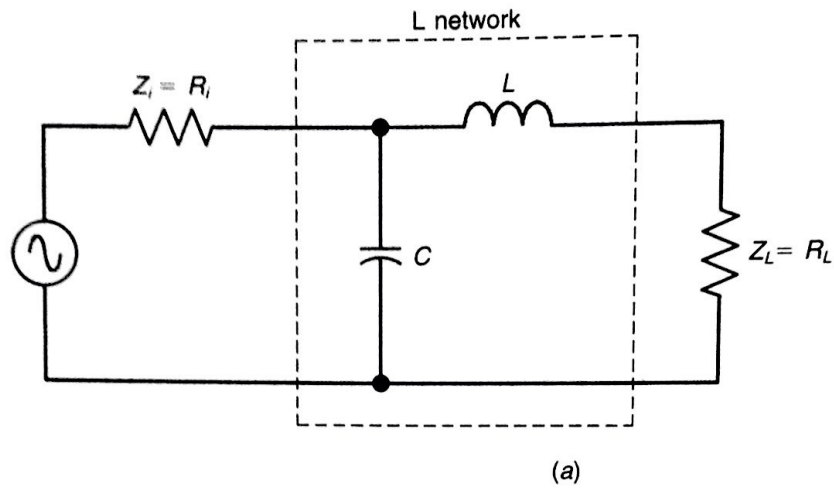


$$X_L = \sqrt{R_i R_L - (R_L)^2}$$

$$Q = \sqrt{\frac{R_i}{R_L} - 1}$$

$$X_C = \frac{R_i R_L}{X_L}$$

$$R_L < R_i$$

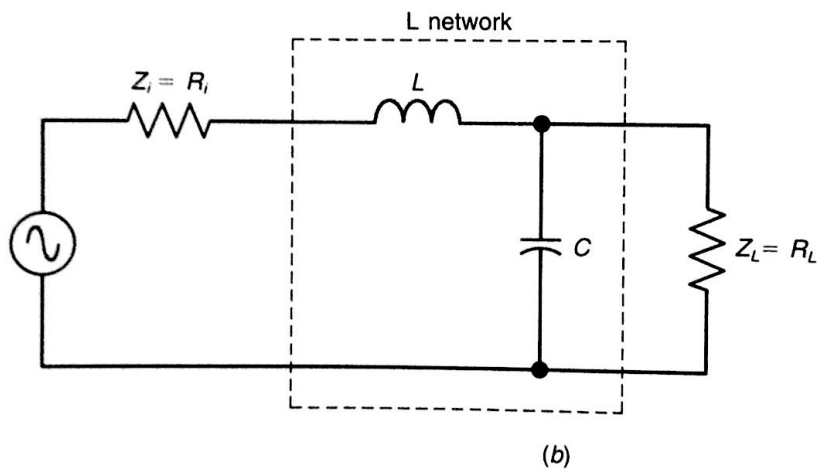

$$X_L = \sqrt{R_i R_L - (R_i)^2}$$

$$Q = \sqrt{\frac{R_L}{R_i} - 1}$$

$$X_C = \frac{R_i R_L}{X_L}$$

$$R_L > R_i$$